

INSTITUTO POLITÉCNICO  
NACIONAL  
ESCUELA SUPERIOR DE CÓMPUTO



INSTRUMENTATION

PRACTICE 2:  
Use of Resistive Sensors

GROUP:  
3CV2

TEACHER:  
ISMAEL CERVANTES DE ANDA

STUDENTS:  
ADAN CARDENAS, ANDREA ABIGAIL  
ROMERO ORTEGA, CHRISTIAN  
BRAVO TORRES, ALEJANDRO

09/02/2019

### Practice Objective:

During the lab practice we may understand how resistive transducers work, and how they can be used with a Wheatstone bridge. It's necessary to understand how resistive transducer works because with them we may measure many measurement units like a tool measurement does.

### Practice Introduction:

First, we need to understand some basic concepts about fundamental parts of the practice.

A Wheatstone bridge is an electrical circuit used to measure an unknown electrical resistance by balancing two legs of a bridge circuit, one leg of which includes the unknown component.

A **potentiometer** is a three-terminal resistor with a sliding or rotating contact that forms an adjustable voltage divider. If only two terminals are used, one end and the wiper, it acts as a variable resistor.

A thermistor is a type of resistor whose resistance is dependent on temperature, more so than in standard resistors. The word is a portmanteau of thermal and resistor.

An **operational amplifier** (often **op-amp**) is a DC-coupled high-gain electronic voltage amplifier with a differential input and, usually, a single-ended output. In this configuration, an op-amp produces an output potential that is typically hundreds of thousands of times larger than the potential difference between its input terminals.

Pin configuration:

- V+: non-inverting input
- V-: inverting input
- Vout: output
- VS+: positive power supply
- VS-: negative power supply


Other types of differential amplifier include the fully differential amplifier (similar to the op-amp, but with two outputs) and the instrumentation amplifier (usually built from three op-amps).

A voltage follower (also called a unity-gain amplifier and a buffer amplifier) is an op-amp (operational amplifier) circuit which has a voltage gain of 1. This means that this op amp does not provide any amplification to the signal. The reason it is called a voltage follower is because the output voltage directly follows the input voltage, meaning the output voltage is the same as the input voltage. Thus, for example, if 10V goes into the op amp as input, 10V comes out as output. A voltage follower acts as a buffer, providing no amplification or attenuation to the signal.
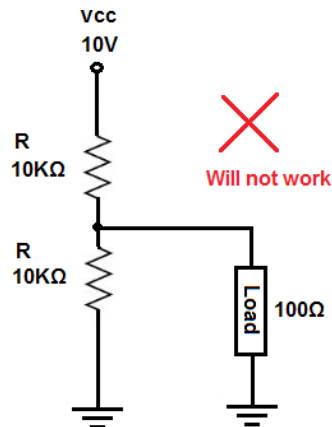
### Voltage Followers are Important in Voltage Divider Circuits

Another reason why voltage followers are used is because of their importance in voltage divider circuits. This again deals with ohm's law. According to ohm's law, voltage = current x resistance ( $V=IR$ ).

In a circuit, voltage divides up or is allocated according to the resistance or impedance of components.



The above circuit will not work, and it will be explained now why not. In the circuit above, we have a voltage divider between the top 10KΩ resistor and the bottom 10KΩ and 100Ω resistors in parallel. The voltage divider equation is characterized by the following equation,  $10K\Omega$  and  $10K\Omega || 100\Omega$ .

Doing the math across the 10KΩ and the 100Ω resistors in parallel gives us,  $10K\Omega || 100\Omega = (10K\Omega)(100\Omega)/1.1K\Omega = 99.01\Omega \sim 99\Omega$ .

So, we next have a voltage divider between the 10KΩ resistor and the 99Ω resistor.


We now can use the voltage divider formula to see how much voltage will fall across the top 10KΩ resistor and the bottom 10KΩ resistor in parallel with the 100Ω resistor.

The voltage divider formula for the voltage across the top 10KΩ resistor is,  $V = 10V(10K\Omega)/(10K\Omega + 99\Omega) = 9.9V$ .

The voltage divider formula for the voltage across the bottom 10KΩ resistor and the 100Ω resistor is,  $V = 10V(99\Omega)/(10,099\Omega) = 0.098V$  or 98mV.

Now let's say the load needs about 5V to operate. You can see based on the calculation, there will not be enough voltage at the output. As we calculated, we had 98mV as our voltage across the load at the output.

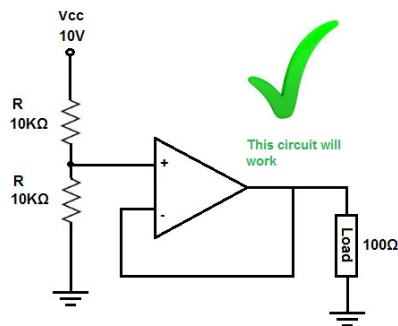Let's see how this circuit changes now with an op amp, with its high input impedance, and the load connected to the output of the op amp.



The circuit above now works.

The voltage divider is now between the top 10KΩ resistor and the 10KΩ resistor and op amp at the bottom.


The op amp virtually offers infinite input impedance (obviously, it's not infinite in real life). Let's assume it's 100MΩ, though it can be much more.

The equation that would characterize our voltage divider is between,  $10K\Omega$  and  $10K\Omega \parallel 100M\Omega$ .

Doing the math on parallel resistance of the  $10K\Omega \parallel 100M\Omega$  resistance gives,  $(10K\Omega)(100M\Omega)/(10K\Omega + 100M\Omega) = 9999\Omega \sim 10K\Omega$ .

Any voltage divider composed of the same 2 resistances gives half the voltage of the power supply. But just to show the math, we have the voltage divider formula,  $10V * (10K\Omega)/(10K\Omega + 10K\Omega) = 5V$ . As we can notice 5 volts falls across the top 10KΩ resistor and 5V falls across the bottom 10KΩ resistor and the 100Ω, because of the 100Ω and 10KΩ resistor are in parallel both receive the same 5V.

## Differential Amplifier

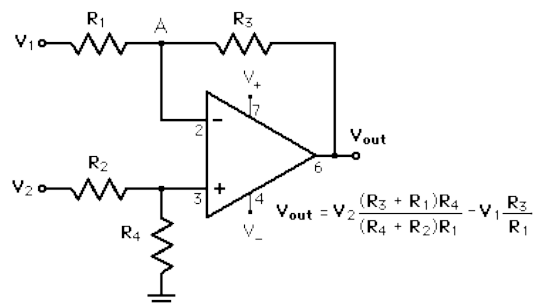

The difference amplifier shown in the above circuit is a combination of both inverting and non-inverting amplifiers. If the non-inverting terminal is connected to ground, the circuit operates as an inverting amplifier.


Usually for a differential amp,  $R3 = R4$  and  $R1 = R2$ .

In that case the coefficients for  $V1$  and  $V2$  are equal and is  $V1 = V2$  (definition of common mode signal) then the output will be zero.

But if there is mismatch between  $R1$  and  $R2$  or between  $R3$  and  $R4$  then the coefficients are different and you get a non zero output when  $V1 = V2$ . The output value/ $V1$  is the common mode rejection ratio. Usually it is small for tight-toleranced resistors and can be expected to be about -60 dB (around 1/1000th) when resistors are matched to  $\pm 0.1\%$ .

## Practice Development:

In part one we needed to build a Wheatstone bridge, but this time instead of using a potentiometer or variable resistor a thermistor was used, the reason was that thermistor will change its resistance value by the time we light the fire close of it. As a result of this, the resistance was going to affect the voltage divider giving us a change in the output voltage number two, which was expected to occur in order to see the changes at the second part of the circuit.

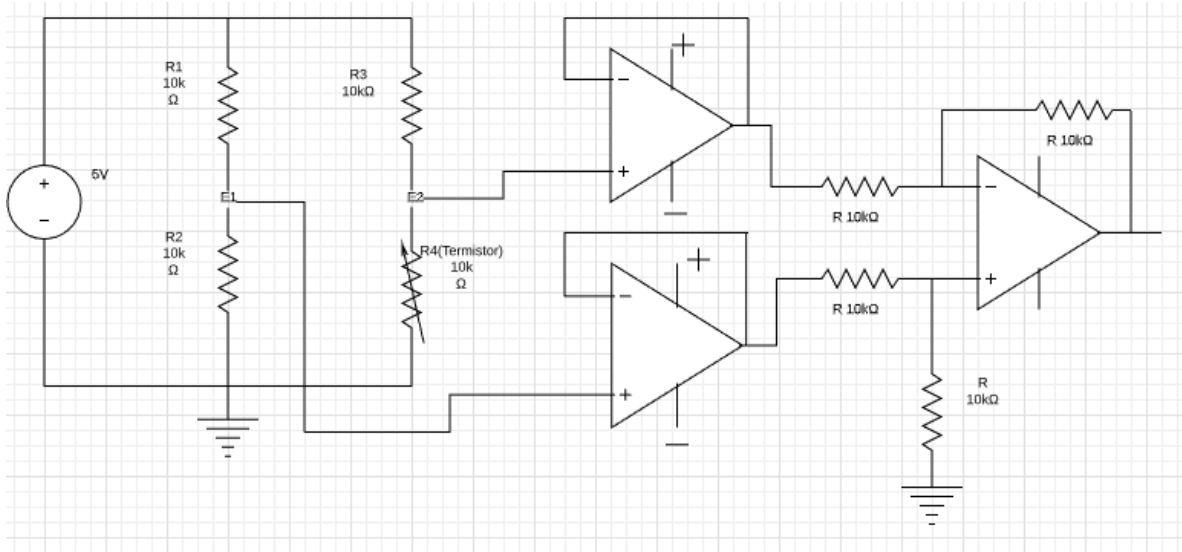

Circuit 1

Once we had finished putting together circuit one we started the making off instrumentation amplifier (second part). As we could see at the introduction the instrumentation amplifier is made of two voltage followers which outputs will be connected into an operational amplifier. The operational amplifier's output will be the result of the voltages difference, and the voltage follower's inputs are the output voltages from part one. As soon as we light the fire the thermistor voltage increments and voltage number two falls.

Table 1. Calculated

Temperature (°C)	E1(V)	E2(V)	E1-E2(V)	Vsal (V)	$\Delta R$ (Ω)	R <sub>sen</sub> (Ω)
91.700	2.500	0.047	2.453	2.4539	-9905.108	94.892
81.500	2.500	0.093	2.407	2.4007	-9810.267	189.733
76.000	2.500	0.202	2.298	2.2865	-9578.991	421.009
74.700	2.500	0.304	2.196	2.1799	-9352.641	647.359
70.700	2.500	0.383	2.117	2.0982	-9170.457	829.543
67.800	2.500	0.466	2.034	2.0087	-8972.210	1027.790
66.300	2.500	0.565	1.935	1.9322	-8726.043	1273.957
61.500	2.500	0.782	1.718	1.7525	-8146.041	1853.959
60.700	2.500	0.830	1.670	1.6833	-8009.592	1990.408
58.800	2.500	0.922	1.578	1.5674	-7739.088	2260.912
56.100	2.500	1.083	1.417	1.4211	-7235.129	2764.871
51.500	2.500	1.365	1.135	1.1262	-6244.842	3755.158
46.000	2.500	1.675	0.825	0.8395	-4962.406	5037.594
43.700	2.500	1.792	0.708	0.7079	-4413.965	5586.035
38.100	2.500	2.049	0.451	0.4554	-3056.591	6943.409
30.600	2.500	2.326	0.174	0.18563	-1301.421	8698.579
29.040	2.500	2.355	0.145	0.1587	-1096.408	8903.592

[illegible]

Temperature (°C)	V <sub>sal</sub> (V)	ΔR (Ω)	R <sub>sen</sub> (Ω)
30.54	0.719	2876.000	12876.000
33.44	1.0334	4133.600	14133.600
43	0.9144	3657.600	13657.600
48.6	1.1479	4591.600	14591.600
51.4	1.2452	4980.800	14980.800
55.2	1.415	5660.000	15660.000
60.4	1.5402	6160.800	16160.800
64.5	2.0587	8234.800	18234.800
70.7	1.8377	7350.800	17350.800
78.5	1.9928	7971.200	17971.200
84.7	2.1099	8439.600	18439.600
85.8	2.1327	8530.800	18530.800

1. *Say what differences the circuits that were used in this practice have.*

For circuit 1 we have an arrangement that implements the Wheatstone Bridge in its first stage, through which, the voltage reading is obtained through resistance variation, a set of OpAmps are used as voltage followers and subtractors, to "clean" the parasitic resistance of our measurements.

On the other hand, in Circuit 2, we have an arrangement with an OpAmp that gives us a voltage measurement, by varying the gain, or controlled gain, by varying the resistance of the sensor in the negative feedback of the OpAmp.

1. Say what differences the circuits that were used in this practice have.

2. Which of the circuits is most advantageous to use? Why?

Circuit no.2, due to its easy construction, its operating range is very similar, its sensing is effective and low cost.

3. How else can measurements be made?

There are at least two usual ways of measuring, with 2 and 4 wires, however, with 2 wires, there are many measurement errors, then we would consider the Kelvin or Four-terminal sensing method.

This method, developed by Lord Kelvin in 1861 [8], is the method used in many ohms and impedance analyzers and consists of using different cables for excitation with the current source and for measurement, so that the voltage drops produced in contacts and in the cables themselves will not be measured by the device. **Fig. 1.** Separation of current and voltage electrodes eliminates the lead and contact resistance from the measurement.

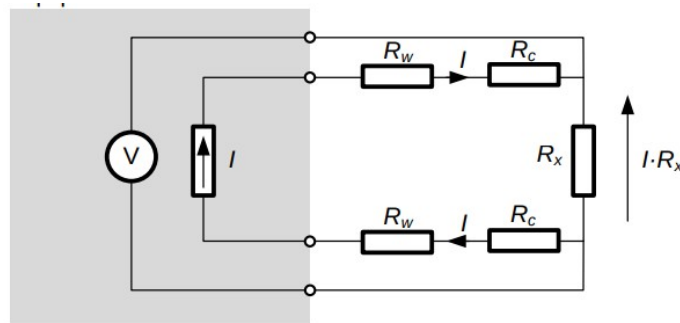



Figure 1: Four-terminal sensing

4. To measure the temperature inside an oven, what transducer would you use?

We could occupy one similar to that of Circuit No.2, with the implementation adjustments, materials and calibration necessary; or by implementing a sensor through a thermocouple. [9]

**Simulations:**

**Circuit No.1**

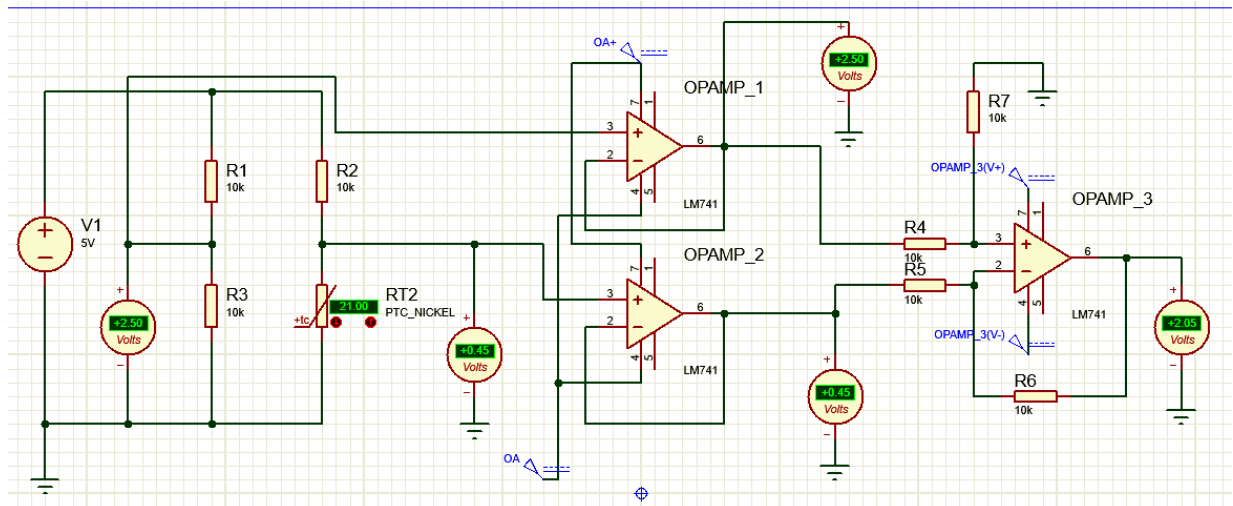

**Sources of information:**

[https://en.wikipedia.org/wiki/Wheatstone\\_bridge](https://en.wikipedia.org/wiki/Wheatstone_bridge)  
<https://en.wikipedia.org/wiki/Potentiometer>  
<https://en.wikipedia.org/wiki/Thermistor>  
<http://www.learningaboutelectronics.com/Articles/Voltage-follower>  
<https://www.allaboutcircuits.com/textbook/semiconductors/chpt-8/building-a-differential-amplifier/>  
<https://www.quora.com/What-will-be-the-CMRR-for-a-differential-amplifier>  
<https://hetpro-store.com/TUTORIALES/amplificador-diferencial/>  
[8] [https://www.academia.edu/29112469/Electrical\\_Conductivity\\_and\\_Resistivity](https://www.academia.edu/29112469/Electrical_Conductivity_and_Resistivity)  
[9] Ioffe, Abraham F.: Semiconductors thermoelements and thermoelectric cooling. Infosearch Ltd., 1956.  
[http://www.infoagro.com/instrumentos\\_medida/doc\\_termometro.asp?k=62](http://www.infoagro.com/instrumentos_medida/doc_termometro.asp?k=62)  
<https://en.wikipedia.org/wiki/Thermocouple>  
[https://es.wikipedia.org/wiki/Detector\\_de\\_calor](https://es.wikipedia.org/wiki/Detector_de_calor)